

# FWC RTL ASSIGNMENT-1

Chirag Shah

## Main Code

```
`timescale 1ns / 1ps
module down_counter(
    input clk,
    input [7:0]in,
    input latch,
    input dec,
    input div_2,
    output reg[7:0] count,
    output reg z_flag
);
always @ (posedge clk)
begin
    if ({latch,dec}==2'b10)
        count <= in;          //same as i/p
    else if ({latch,dec}==2'b11)
        count <=in;          //same as i/p since latch is high
    else if({latch,dec}==2'b01)
        begin
            if (count!=0)
            begin
                count<=count-1;      //decrements since dec is high and latch is 0
                z_flag<=0;          // when count !=0 zero flag is low
            end
        end
    else
```

```

    z_flag<=1;          // when count = 0 zero flag is high
end
else if({latch,dec}==2'b00 & div_2==1)
count<=count/2;        //result will be div/2 since div_2 is high
else
count<=count;
end
endmodule

```

## Test bench

```

`timescale 1ns / 1ps
module down_counter_tb;

reg clk,latch,dec,div_2;
reg [7:0] in=8'b00010000;

wire [7:0] count;
wire z_flag;


down_counter u1(.clk(clk),.in(in),.latch(latch),
               .dec(dec),.div_2(div_2),.count(count),.z_flag(z_flag));

always #5 clk=~clk;
initial begin
clk<=0;
#10 latch<=1;dec<=0;
#10 latch<=0;dec<=1;div_2=0;
#10 latch<=0;dec<=1;div_2=0;
#10 latch<=0;dec<=0;div_2=1;


```

```
#10 latch<=0;dec<=1;div_2=0;  
#10 latch<=0;dec<=0;div_2=1;  
#10 latch<=0;dec<=1;div_2=0;  
#50 $stop;  
end  
endmodule
```


## Device Diagram

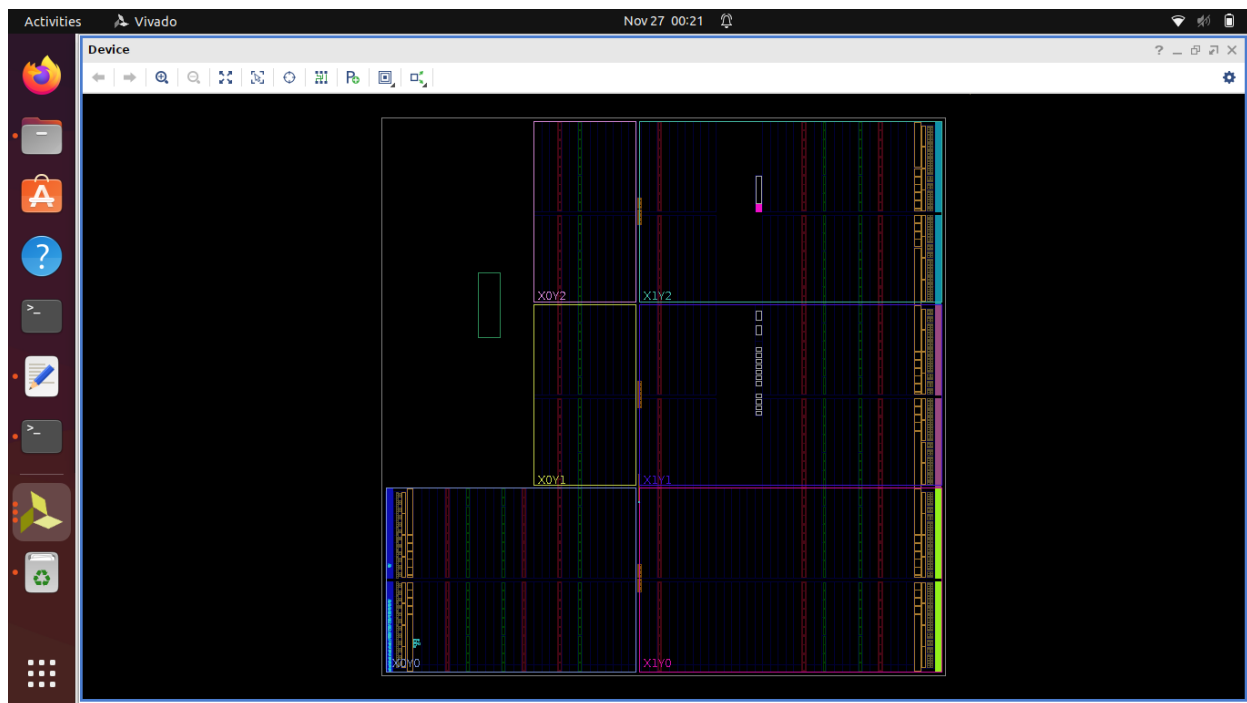

## Timing Diagram

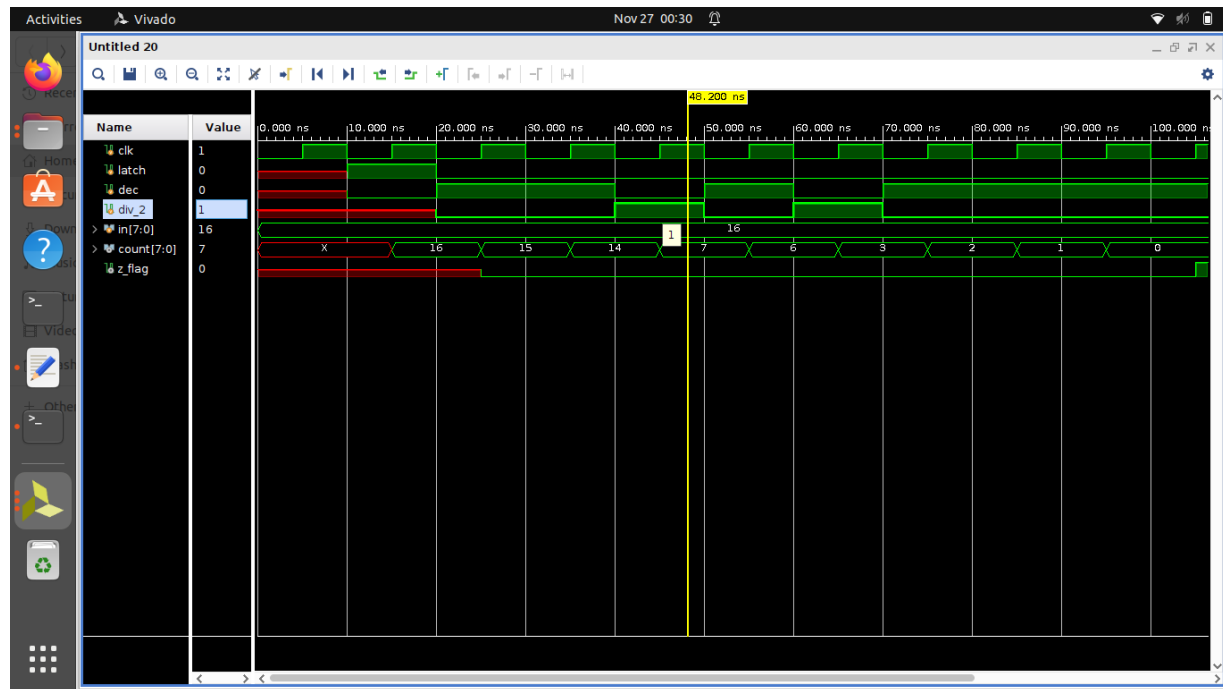

## Schematic Diagram

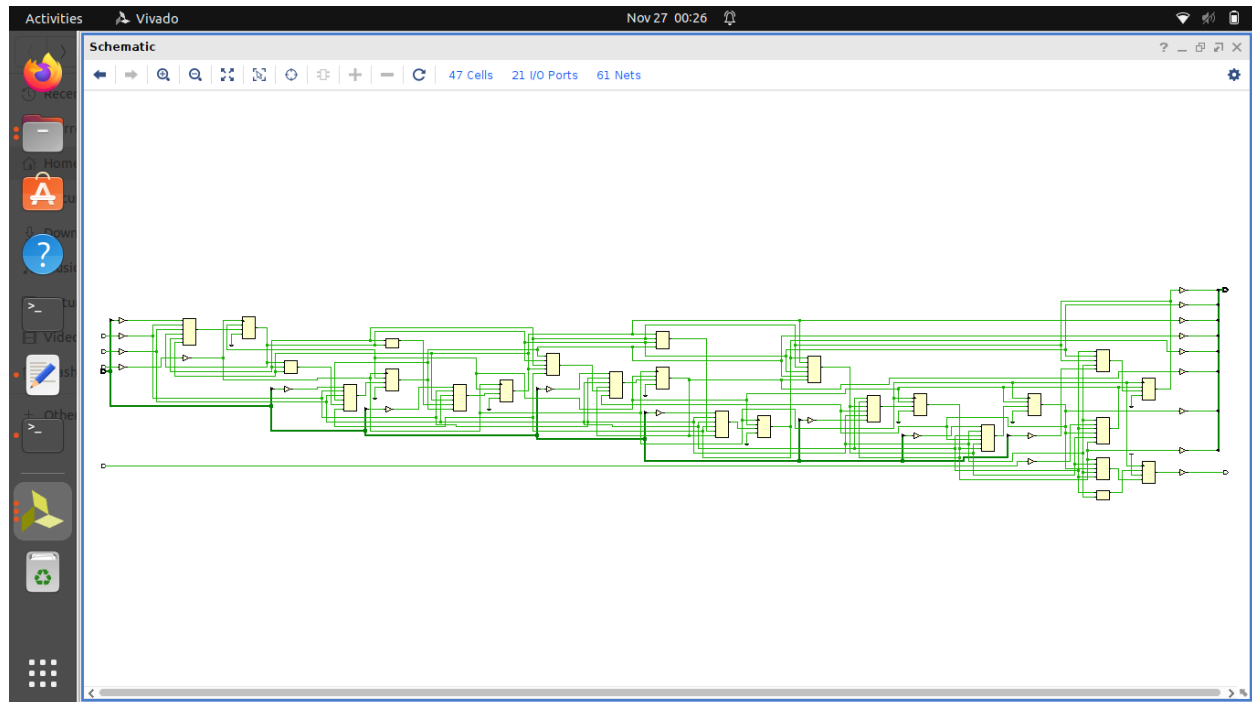

## Dataflow Design (netlist)

